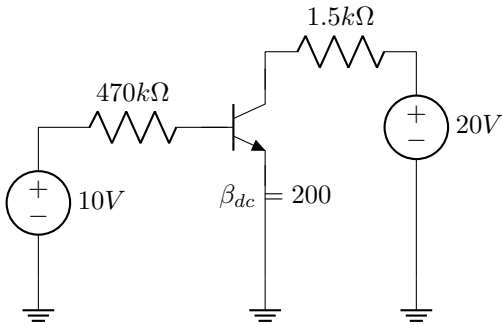


Bipolar Junction Transistors

Jiwook Kim

Question 1. A transistor circuit has a collector supply voltage of 20V, a collector resistance of $1.5k\Omega$, and a collector current of 6mA, what is the collector emitter voltage?



Using kirchoff voltage law

$$20V - I_c * 1.5k\Omega - V_{CE} = 0$$

$$20V - 1.5k\Omega * 6mA = V_{CE}$$

$$20V - 9V = V_{CE}$$

$$V_{CE} = 11V$$

Question 2 If a transistor has a collector current of 100mA and a collector-emitter voltage of 3.5V, what is its power dissipation

$$\text{Collector current} = I_c = 100mA$$


$$V_{CE} = 3.5V$$

$$P = I_c * V_{CE}$$

$$P = 100mA * 3.5V$$

$$P = 350mW$$

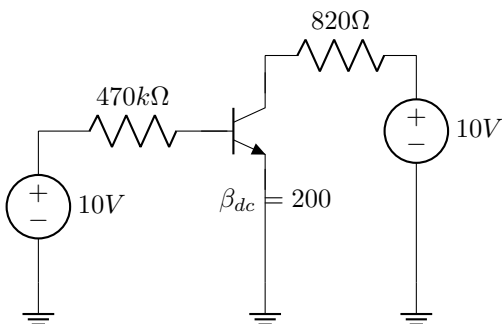Question 3 What are the collector -emitter voltage and the transistor power dissipation? (Give Answers for the ideal and the second approximation)



Ideal approximation

Using kirchoff's Voltage law

$$10V - 470k\Omega * I_b = 0$$

$$I_b = 21.3\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 200 * 21.3\mu A$$

$$I_c = 4.26mA$$

$$V_{CE} = 10V - 820\Omega * I_c$$

$$V_{CE} = 10V - 820\Omega * 4.26mA$$

$$V_{CE} = 6.51V$$

$$P_{CE} = V_{CE} * I_c$$

$$P_{CE} = 6.51V * 4.26mA$$

$$P_{CE} = 27.8mW$$

Second approximation

Using kirchoff's Voltage law

$$10V - 470k\Omega * I_b = 0$$

$$I_b = (10V - V_{be}) / 470k\Omega$$

Assuming $V_{be} = 0.7V$

$$I_b = (10V - 0.7V) / 470k\Omega$$

$$I_b = 19.8\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 200 * 19.8\mu A$$

$$I_c = 3.96mA$$

$$V_{CE} = 10V - 820\Omega * I_c$$

$$V_{CE} = 10V - 820\Omega * 3.96mA$$


$$V_{CE} = 6.76V$$

$$P_{CE} = V_{ce} * I_c$$

$$P_{CE} = 6.76V * 3.96mA$$

$$P_{CE} = 26.77mW$$

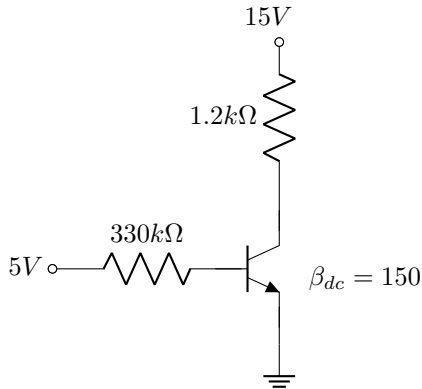Question 4 Circuit below shows a simpler way to draw a transistor circuit it works the same as the circuits already discussed. What is collector-emitter voltage? The transistor power dissipation?(give answer for the ideal and the second approximation



Ideal approximation

Using kirchhoff's Voltage law

$$5V - 330k\Omega * I_b = 0$$

$$I_b = 15.15\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 150 * 21.3\mu A$$

$$I_c = 2.27mA$$

$$V_{CE} = 15V - 1.2k\Omega * I_c$$

$$V_{CE} = 15V - 1.2k\Omega * 2.27mA$$

$$V_{CE} = 12.3V$$

$$P_{CE} = V_{CE} * I_c$$

$$P_{CE} = 12.3V * 2.27mA$$

$$P_{CE} = 27.9mW$$

Second approximation

Using kirchhoff's Voltage law

$$I_b = (10V - V_{be}) / 330k\Omega$$

Assuming $V_{be} = 0.7V$

$$I_b = (10V - 0.7V) / 330k\Omega$$

$$I_b = 13\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 150 * 13\mu A$$

$$I_c = 1.95mA$$

$$V_{CE} = 10V - 1.2k\Omega * I_c$$

$$V_{CE} = 10V - 1.2k\Omega * 1.95mA$$


$$V_{CE} = 12.7V$$

$$P_{CE} = V_{ce} * I_c$$

$$P_{CE} = 12.7V * 1.95mA$$

$$P_{CE} = 24.7mW$$

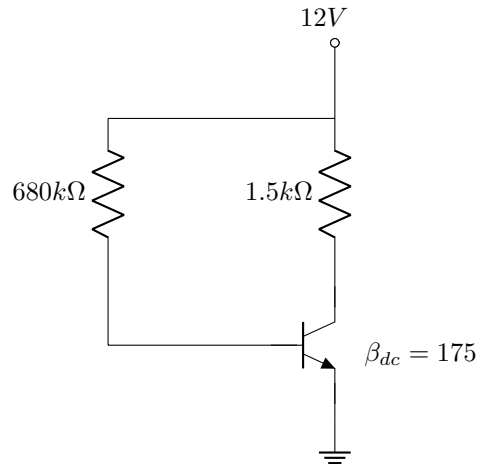Question 5. When the base and collector supplies are equal, the transistor can be drawn as shown in below. What is the collector-emitter voltage in this circuit? the transistor power? (Give answers for the ideal and the second approximation)



Ideal approximation

Using kirchhoff's Voltage law

$$12V - 680k\Omega * I_b = 0$$

$$I_b = 17.65\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 175 * 17.65\mu A$$

$$I_c = 3.1mA$$

$$V_{CE} = 12V - 1.5k\Omega * I_c$$

$$V_{CE} = 12V - 1.5k\Omega * 3.1mA$$

$$V_{CE} = 7.35V$$

$$P_{CE} = V_{ce} * I_c$$

$$P_{CE} = 7.35V * 3.1mA$$

$$P_{CE} = 22.79mW$$

Second approximation

Using kirchhoff's Voltage law

$$I_b = (12V - V_{be}) / 680k\Omega$$

Assuming $V_{be} = 0.7V$

$$I_b = (12V - 0.7V) / 680k\Omega$$

$$I_b = 16.62\mu A$$

$$I_c = \beta * I_b$$

$$I_c = 175 * 16.62\mu A$$

$$I_c = 2.91mA$$

$$V_{CE} = 12V - 1.5k\Omega * I_c$$

$$V_{CE} = 12V - 1.5k\Omega * 2.91mA$$

$$V_{CE} = 7.64V$$

$$P_{CE} = V_{CE} * I_c$$

$$P_{CE} = 7.64V * 2.91mA$$

$$P_{CE} = 22.23mW$$

Question 6 What is the current gain of a transistor with a dc alpha of 0.994?

$$\alpha = \beta / (\beta + 1)$$

$$0.994 = \beta / (\beta + 1)$$

$$(\beta + 1) * 0.994 = \beta$$

$$0.994 * \beta + 0.994 = \beta$$


$$0.994 = (1 - 0.994) * \beta$$

$$0.994 / (1 - 0.994) = \beta$$

$$\beta = 165.66$$

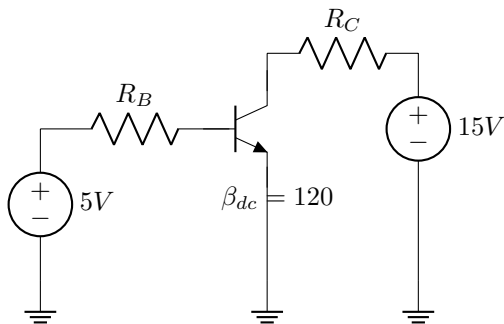Question 7 Design a CE circuit to meet these specifications:

$$V_{bb} = 5V, V_{CC} = 15V, H_{FE} = 120, I_C = 10mA, V_{CE} = 7.5V$$



$$\text{If } I_C = 10mA$$

$$I_C = \beta * I_b = 10mA$$

$$I_b = I_C / 120 = 83.33\mu A$$

Using kirchoff's voltage law.

$$5V - I_b * R_b - 0.7V = 0$$

$$5V - 83.33\mu A * R_b - 0.7V = 0$$

$$R_b = 4.3V / 83.33\mu A = 51.6k\Omega$$

Using kirchoff's voltage law.


$$15V - I_C * R_C - V_{CE} = 0$$

$$(15V - V_{CE}) / I_C = R_C$$


$$(15V - 7.5V) / 10mA = R_C$$

$$(15V - 7.5V) / 10mA = R_C$$

$$R_C = 750\Omega$$

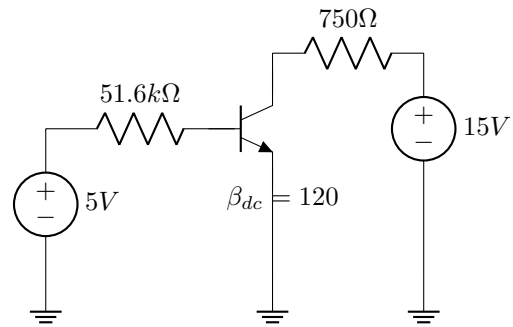

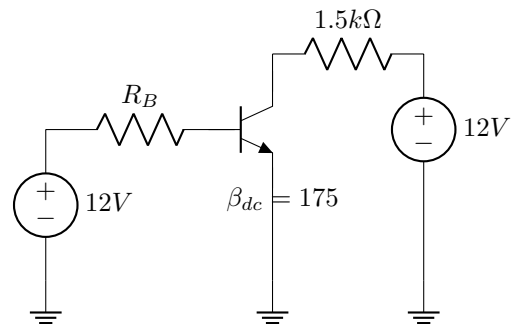Question 8 In the Circuit below, what value base resistor would be needed so $V_{CE} = 6.7V$



$$(12V - V_{CE}) / R_C = I_C$$

$$(12V - 6.7V) / R_C = I_C$$

$$I_C = (12V - 6.7V) / 1.5k\Omega = 3.533mA$$

$$I_C = \beta * I_B$$

$$I_B = I_C / \beta = 3.533mA / 175 = 20.1\mu A$$

$$12V - I_B * R_B - V_{BE} = 0$$

$$11.3 / I_B = R_B$$

$$R_B = 11.3 / 20.1\mu A = 559k\Omega$$

Question 9 A 2N3904 has a power rating of 350 mW at room temperature (25 C). If the collector-emitter voltage is 10V, what is the maximum current that the transistor can handle for an ambient temperature of 50C.

The change in temperature is 50C - 25C which is 25C.

derating factor is (5 mW/C)

The change in temperature is 25C

Thus (5 mW/C) * 25C = 125mW

Subtracting the difference in power rating in 25C

$$350 mW - 125mW = 225mW$$

Thus, The power rating of 2N3904 at ambient temperature 50C is 225mW


knowing that $V_{CE} * I = P$

$$10V * I = 225mW$$

$$I = 22.5\text{mA}$$

Thus maximum current that the transistor can handle for an ambient temperature of 50°C is 22.5mA

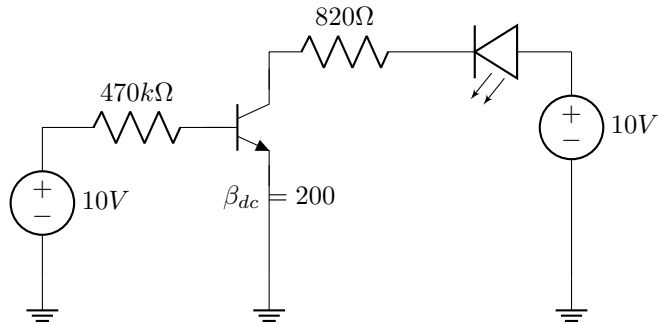Question 10 Suppose we connect an LED in series with the 820Ω of Fig 6-20. What does the LED current equal?



$$I_b = (10\text{V} - V_{be}) / 470\text{k}\Omega$$

Assuming $V_{be} = 0.7\text{V}$

$$I_b = (10\text{V} - 0.7\text{V}) / 470\text{k}\Omega$$

$$I_b = 19.8\text{ }\mu\text{A}$$

$$I_c = \beta * I_b$$

$$I_c = 200 * 19.8\text{ }\mu\text{A}$$

$$I_c = 3.96\text{mA}$$

Thus, LED current equals to 3.96mA

$$I_c = (20\text{V} - 0) / 3.3\text{k}\Omega$$


$$I_c = 6.06\text{mA at } V_{CE} = 0$$

To find collector-emitter voltage at the cutoff point, substitute I_c to 0.


$$I_c = (20\text{V} - V_{CE}) / 3.3\text{k}\Omega$$

$$0 = (20\text{V} - V_{CE}) / 3.3\text{k}\Omega$$

$$V_{CE} = 20\text{V at } I_c = 0$$

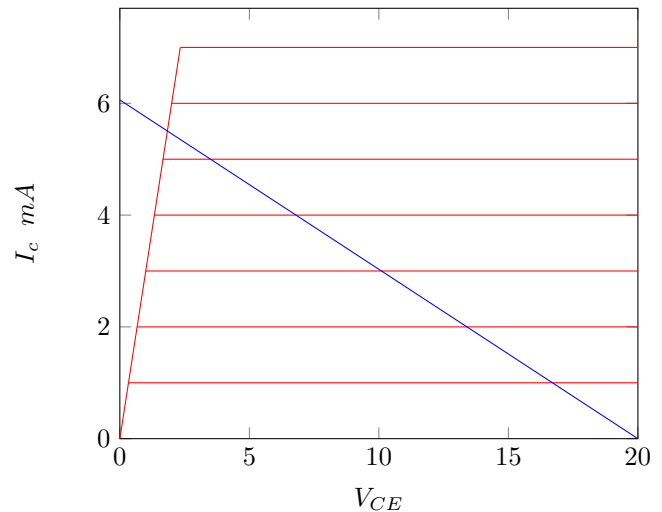

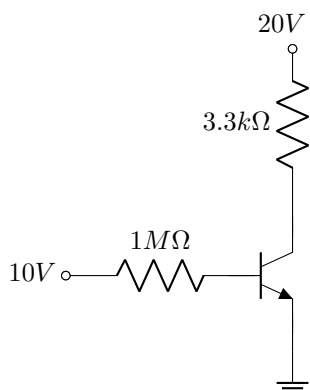Question 11 Draw the load line for Circuit below. What is the collector current at the saturation point? The collector - emitter voltage at the cutoff point?




Using Kirchhoff's voltage law

$$20\text{V} - I_c * 3.3\text{k}\Omega - V_{CE} = 0$$

$$I_c = (20\text{V} - V_{CE}) / 3.3\text{k}\Omega$$

To find collector current at saturation point. substitute V_{CE} to 0.

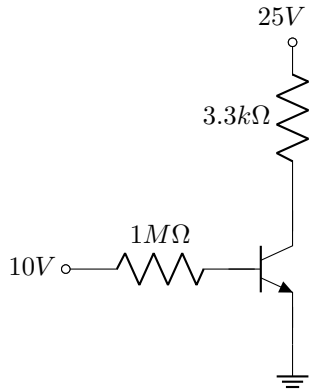Question 12 If the collector supply voltage is increased to 25V in the circuit below, what happens to the load line?



Using Kirchhoff's voltage law

$$25 - I_c * 3.3k\Omega - V_{CE} = 0$$

$$I_c = (25V - V_{CE}) / 3.3k\Omega$$

To find collector current at saturation point, substitute V_{CE} to 0.

$$I_c = (25V - 0) / 3.3k\Omega$$


$$I_c = 7.57mA \text{ at } V_{CE} = 0$$

To find collector-emitter voltage at the cutoff point, substitute I_c to 0.

$$I_c = (25V - V_{CE}) / 3.3k\Omega$$


$$0 = (25V - V_{CE}) / 3.3k\Omega$$

$$V_{CE} = 25V \text{ at } I_c = 0$$

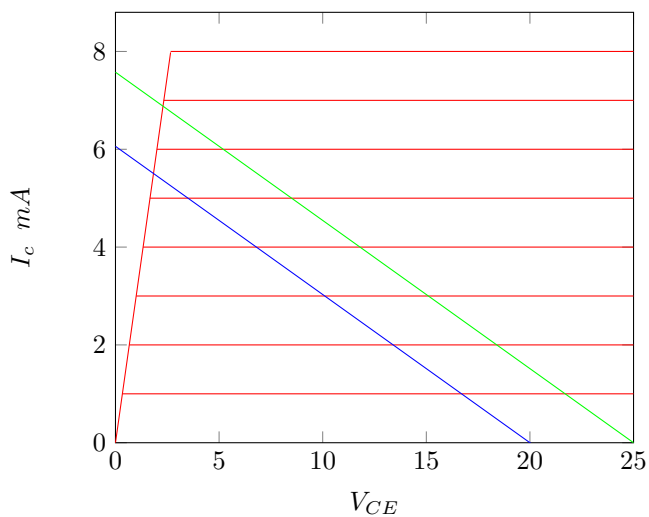

As the collector supply voltage increases, the collector current at saturation point and the collector emitter voltage at the cutoff point increases.

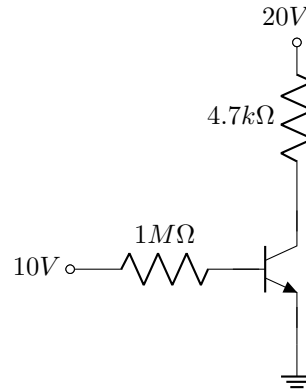Question 13 If the collector resistance is increased to 4.7 kΩ in the Circuit Below, what happens to the load line?



Using Kirchhoff's voltage law

$$20 - I_c * 4.7k\Omega - V_{CE} = 0$$

$$I_c = (20V - V_{CE}) / 4.7k\Omega$$

To find collector current at saturation point, substitute V_{CE} to 0.

$$I_c = (20V - 0) / 4.7k\Omega$$


$$I_c = 4.25mA \text{ at } V_{CE} = 0$$

To find collector-emitter voltage at the cutoff point, substitute I_c to 0.

$$I_c = (20V - V_{CE}) / 4.7k\Omega$$


$$0 = (20V - V_{CE}) / 4.7k\Omega$$

$$V_{CE} = 20V \text{ at } I_c = 0$$

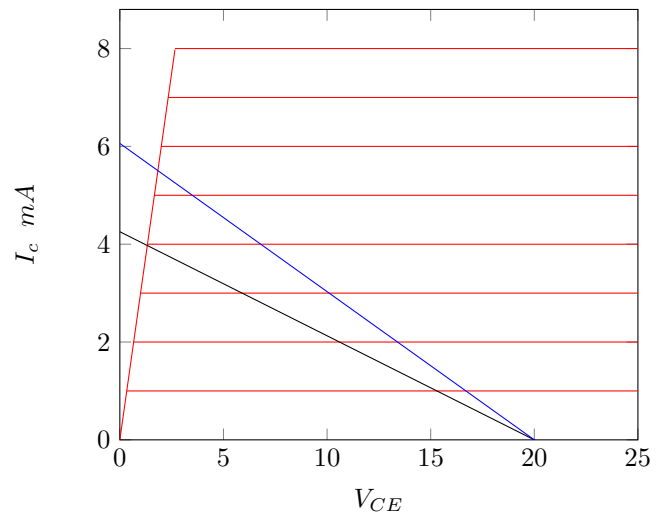

As the collector resistance increase, the slope of load line decreases.

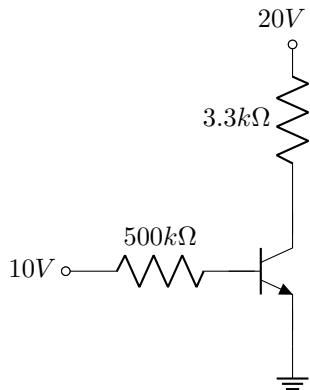Question 14. As the base resistance of is reduced to 500kΩ. What happens to the load line?



Using Kirchhoff's voltage law

$$20 - I_c * 3.3k \Omega - V_{CE} = 0$$

$$I_c = (20V - V_{CE}) / 3.3k\Omega$$

To find collector current at saturation point. substitute V_{CE} to 0.

$$I_c = (20V - 0) / 3.3k\Omega$$


$$I_c = 6.06mA \text{ at } V_{CE} = 0$$

To find collector-emitter voltage at the cutoff point, substitute I_c to 0.

$$I_c = (20V - V_{CE}) / 3.3k\Omega$$


$$0 = (20V - V_{CE}) / 3.3k\Omega$$

$$V_{CE} = 20V \text{ at } I_c = 0$$

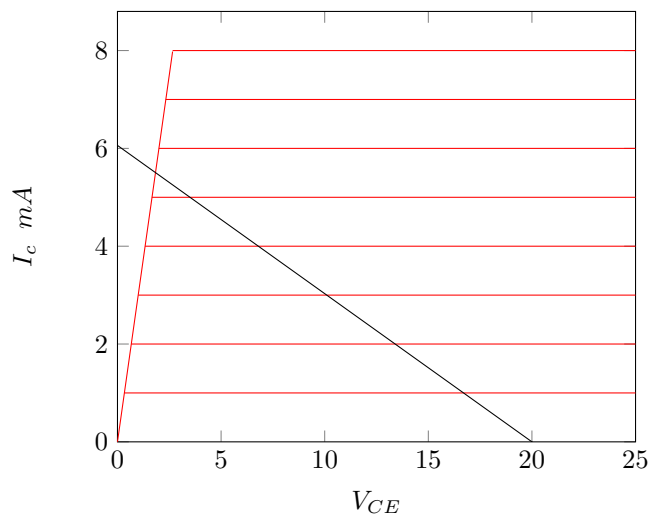

As the base resistance change, the load line does not change.

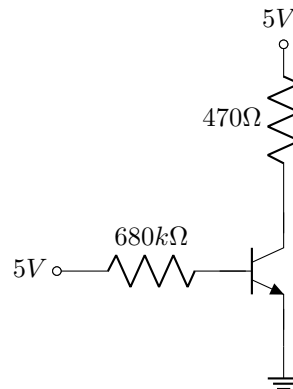Question 15 Draw the load line for circuit below. What is the collector current at the saturation point? The collector - emitter voltage at the cut off point?



Using Kirchhoff's voltage law

$$5V - I_c * 470\Omega - V_{CE} = 0$$

$$I_c = (5V - V_{CE}) / 470\Omega$$

To find collector current at saturation point. substitute V_{CE} to 0.

$$I_c = (5V - 0) / 470\Omega$$

$$I_c = 10.64mA \text{ at } V_{CE} = 0$$

To find collector-emitter voltage at the cutoff point, substitute I_c to 0.

$$I_c = (5V - V_{CE}) / 470\Omega$$

$$0 = (5V - V_{CE}) / 470\Omega$$

$$V_{CE} = 5V \text{ at } I_c = 0$$

