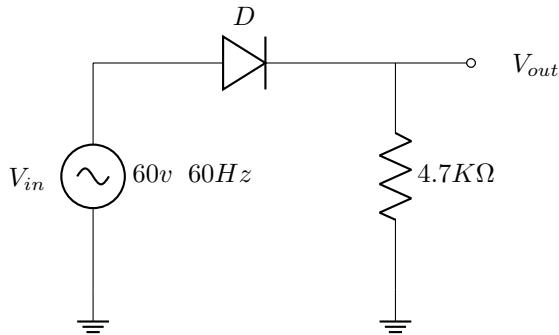


# Diode Circuit

Jiwook Kim

**Question 1.** What is the peak output voltage if the diode is ideal? The average value? the dc Value? sketch

**Answer to Question 1**



Assuming diode is Ideal

$$V_{rms} = V_p / \sqrt{2} \text{ Since it is forward biased}$$

$$V_{pp} = V_{rms} * \sqrt{2}$$

$$V_{pp} = 60V * \sqrt{2}$$

$$V_{pp} = 70.71V, \text{ Peak load voltage} = 70.71V$$

Average value of diode, or DC value of Half wave Signal

$$V_{dc} = V_{pp} / \pi = 70.71V / \pi = 22.50V$$


$$f_{out} = f_{in} \text{ for half wave signal}$$

$$\omega = 2 * \pi * f = 2 * \pi * 60Hz$$

$$V_{in} = V_{pp} * \sin(2 * \pi * f * t)$$


Since only positive part of the AC voltage is affect for  $V_{out}$

$V_{out}$  to time graph

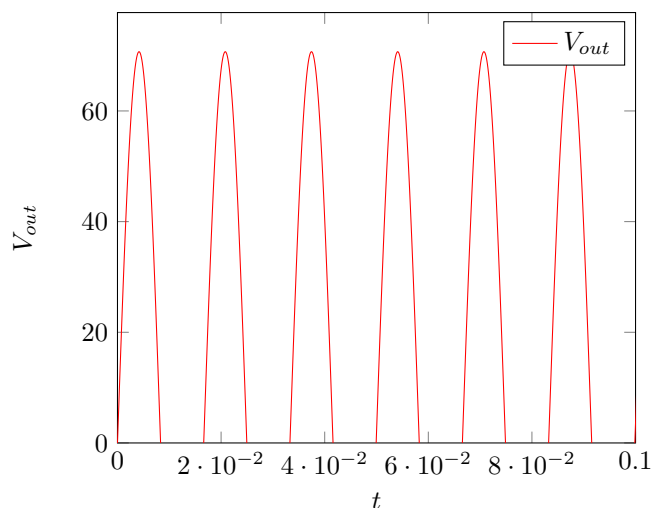

**Question 2.** What is the peak output voltage below if the diode is ideal? The average value? the dc Value? sketch

**Answer to Question 2**

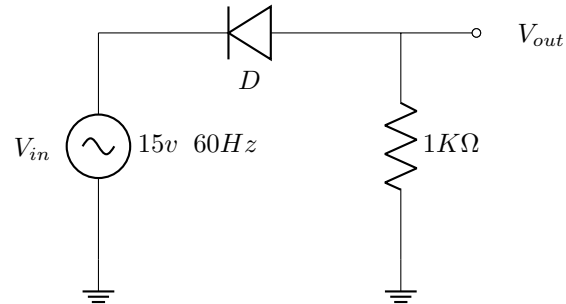

Assuming diode is Ideal

$$V_{rms} = -V_p / \sqrt{2} \text{ (Considering it is reversed bias)}$$

$$V_p = -V_{rms} * \sqrt{2}, V_p = -15V * \sqrt{2}$$

$$V_p = -21.21V, \text{ Peak load voltage} = -21.21V$$

Average value of diode, or DC value of Halfwave Signal

$$V_{dc} = V_p / \pi = -21.21V / \pi = -6.75V$$


$$f_{out} = f_{in} \text{ for half wave signal}$$

$$\omega = 2 * \pi * f = 2 * \pi * 60Hz$$

$$V_{in} = V_p * \sin(2 * \pi * f * t)$$

Since only negative part of the AC voltage is affect for  $V_{out}$

$V_{out}$  to time graph

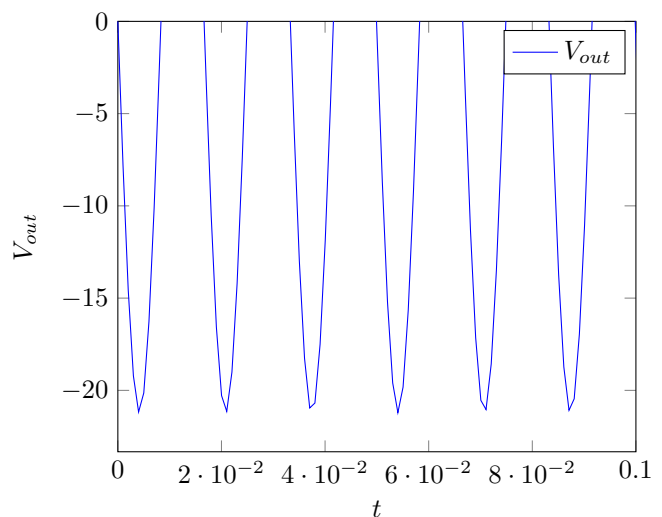

**Question 3** . If a transformer has a turn ratio of 6:1,  $N_1:N_2 = 6:1$  what is the turns secondary voltage? The peak secondary voltage? Assume a primary voltage of  $120V_{rms}$

#### Answer to Question 3

Since the transformer has turn ratio of 6:1, the secondary voltage is  $120V_{rms}/6$ , which is  $20V$ .

The peak voltage is  $20V \cdot \sqrt{2}$  which is  $28.3V$

**Question 4** . A center-tapped transformer with 120 V input has a ratio of 4:1. What is the terms voltage across the upper half of the secondary winding? The peak voltage? What is the terms voltage across the lower half of the secondary winding?

#### Answer to Question 4

Since the transformer has  $N_1:N_2 = 4:1$ ,  $V_1 = 120V$   
4:1 the secondary voltage is  $120V_{rms}/4$ , which is  $30V$ .

Upper half of the secondary winding is half of the rms secondary voltage.

$$V_2 = V_{secondary}/2 = 30V/2 = 15V$$


The rms voltage across upper half of secondary winding is  $V_2 = 15V$

The peak voltage is

$$V_{pp} = V_{rms} \cdot \sqrt{2} = 15 \cdot \sqrt{2} = 21.21V$$

**Question 5** . What is the peak output voltage in Fig. 4-38 if the diodes are ideal? The average value? The dc value? Sketch the output waveform.

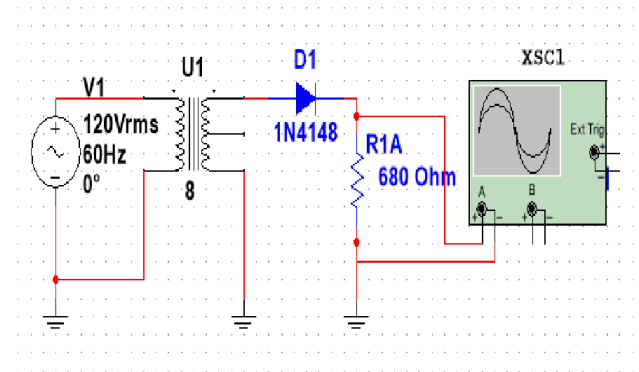**Question 6**. Repeat the preceding problem using the second approximation.



#### Answer to Question 5

##### Ideal diode

Because transformer has turn ratio of  $N_1:N_2 = 8:1$ , secondary voltage ( $V_2$ ) is  $V_1/8$

$$V_2 = V_1/8 = 120V/8 = 15V$$

$$\text{Peak secondary voltage} = V_{secondpp} = 15V \cdot \sqrt{2} = 21.216V$$

$$V_{dc} = V_l/\pi = 21.22V/\pi = 6.754537V$$

#### Answer to Question 6

##### Second approximation model

Voltage drop across diode =  $0.7V$


$$V_2 = V_1/8 = 15V$$

$$\text{Peak of secondary voltage } V_{secondpp} = 15V \cdot \sqrt{2} = 21.216V$$

$$\text{Because of diode } V_l = 21.22V - 0.7V = 20.52V$$

$$V_{dc} = V_l/\pi = 20.52V/\pi = 6.535V$$

##### Oscilloscope Output

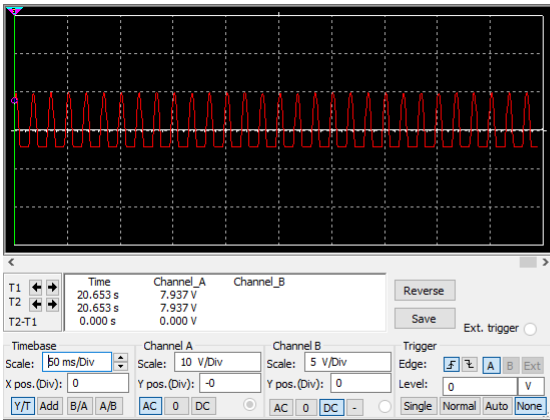

**Question 7.** A half-wave signal with a peak of 20V is the input to a choke-input filter. If  $X_L = 1K\Omega$  and  $X_c = 25\Omega$ , what is the approximate peak to peak ripple across the capacitor?


### Answer to Question 7

$$\begin{aligned} V_p &= 20V \\ X_L &= 1K\Omega \\ X_c &= 25\Omega \\ V_L &= 20V \end{aligned}$$

The circuit acts as voltage divider circuit

$$\begin{aligned} V_c &\approx V_L * X_c / X_L \\ V_c &= 20V * 25 / 1000 \\ V_c &= 0.5V \\ V_c &= 0.5V \text{ peak to peak ripple voltage across the capacitor} \end{aligned}$$

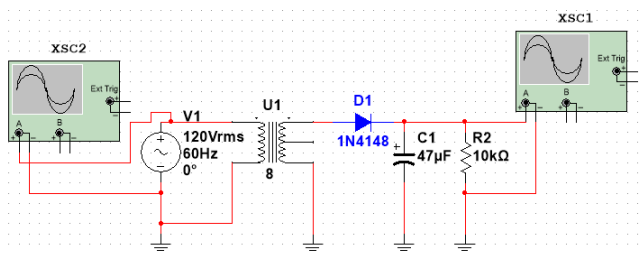**Question 8** .What is the dc output voltage and ripple in below? Sketch the output waveform.



### Answer to Question 8

$$V_1 = 120V$$

$$\begin{aligned} N_1 : N_2 &= 8:1 \\ R_L &= 10k\Omega \\ C &= 47\mu F \end{aligned}$$

Rms secondary voltage

$$V_2 = N_2 / N_1 * V_1 = 1/8 * 120 = 15V$$

$$V_p = V_2 * \sqrt{2} = 15V * \sqrt{2} = 21.21V$$

Assuming diode is ideal,  $V_p = V_{out} = V_L = 21.21V$


Dc load current is needed for calculating peak to peak voltage

$$I_L = V_L / R_L = 21.21V / 10k\Omega = 2.12mA$$


The ripple formula for capacitor-input filter approximating ripple voltage.

$$\begin{aligned} \text{Ripple voltage} &\approx I_L * x_c = 2.12mA * 1/(60Hz * 47\mu F) \\ V_L &= 752mV \text{ peak to peak} \end{aligned}$$

### DC Output Voltage

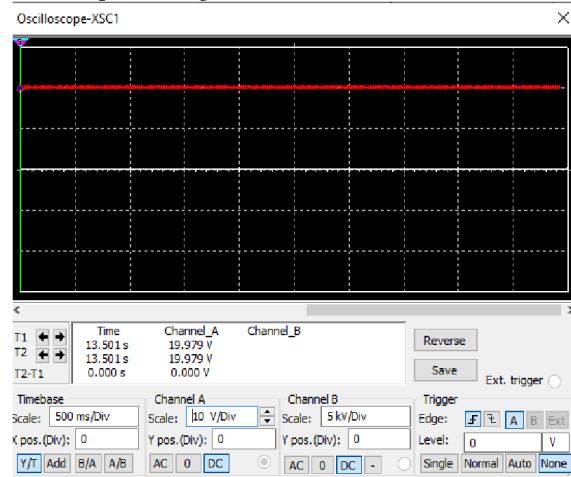


### Ripple voltage Peak to peak

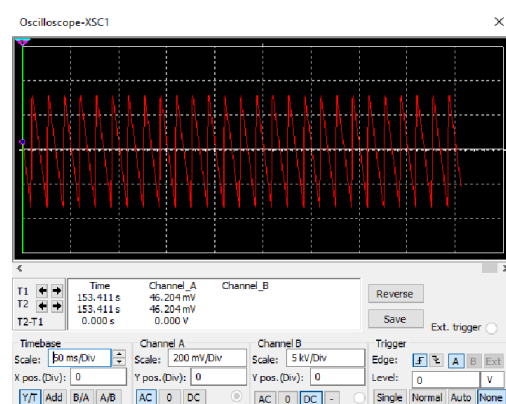

**Question 9** Calculate the dc output voltage and ripple

**Answer to Question 9**

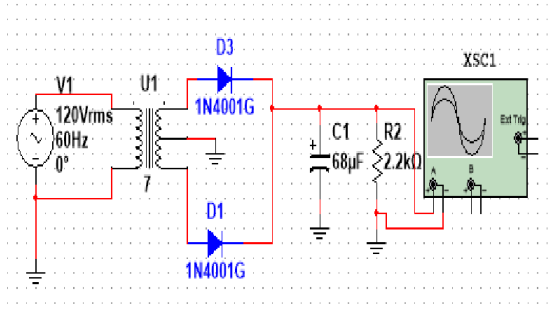

For calculations

$$V_1 = 120V$$

$$N_1 : N_2 = 7:1$$

$$R_L = 2.2k\Omega$$

$$C = 68\mu F$$

rms secondary voltage

$$V_2 = N_2/N_1 * V_1 = 1/7 * 120 = 17.14V$$

$$V_p = V_2 * \sqrt{2} = 24.24V$$

Assuming diode is ideal, and for Full wave rectifier, half of this voltage is input to each half wave section. Assuming small ripple and ideal diode.

$$V_l = V_p/2 = 12.12V$$

Dc load current is needed for calculating peak to peak voltage


$$I_l = V_l / R_L = 12.12V / 2.2k\Omega = 5.5mA$$

The ripple formula for capacitor-input filter approximating ripple voltage.


$$\text{Ripple voltage} \approx I_l / f * C = 5.5mA * 1/(120Hz * 68\mu F)$$

$$V_l = 1.35V \text{ peak to peak}$$

Oscilometer output

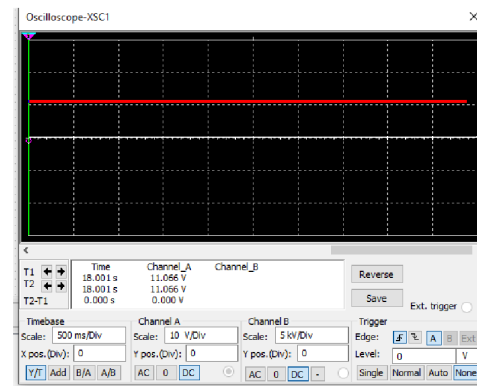

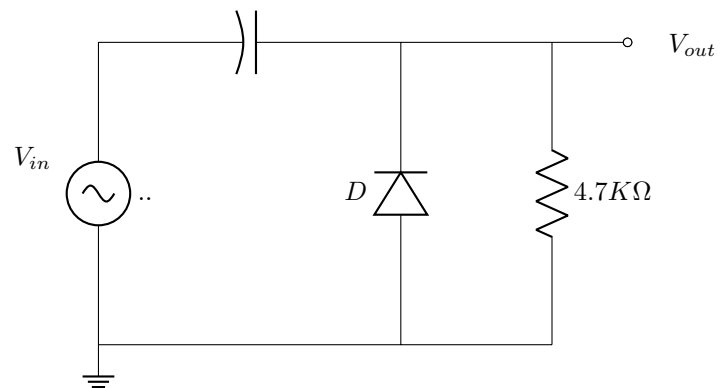**Question 10** Sketch the output waveform. What is the maximum positive voltage? The maximum negative?



**Answer to Question 10**

**Positive clamper Circuit**

Clamper adds a DC voltages to the signal. The positive clamper shifts the ac reference level up to a dc level. An AC source drives the input side of the clamper. The thevenin voltage of the clamper output is the superposition of a dc source and an ac source. The ac signal has a dc voltage  $V_p$  added to it.

Assuming diode is ideal

On the first negative half cycle of input voltage, the diode turns on. at the negative peak voltage the capacitor has fully charged 15V with polarity reversed. then the capacitor retains almost all of its charge of its charge during subsequent cycles.


Beyond negative voltage, the diode turns off. at this time the capacitor remains fully charged. the output voltage will appear as 30V using superposition. than  $v_{out} = 30V$ , and 0V when it is negative cycle. this is because all the current

goes through diode when it is negative cycle.


Thus, minimum voltage would be 0V and maximum voltage would be 30V
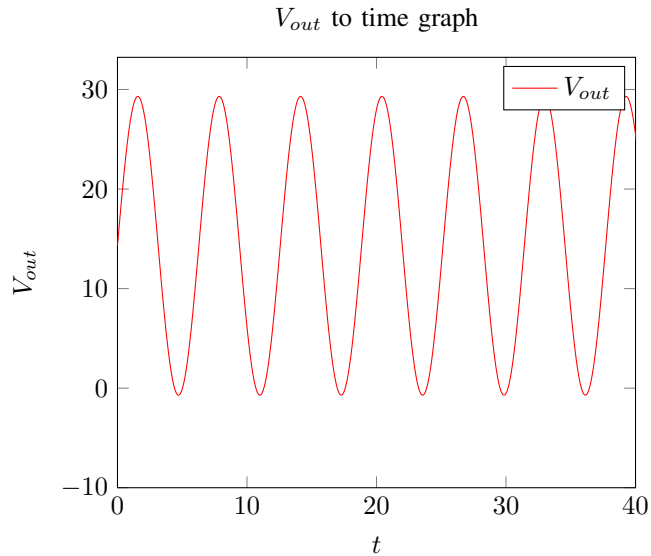
### Real Diode

Since the diode drops 0.7V when conducting, the capacitor voltage does not quite reach  $v_p$ . For this reason clamper is not perfect and the negative peaks have a reference level of -0.7V



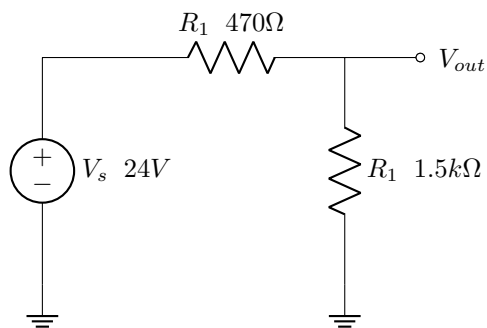
**Question 11** If the zener diode is disconnected, what is the load voltage.




**Answer to Question 11**

$$V_{out} = V_{in} * R_L / (R_1 + R_L) = 24V * 1.5k\Omega / (470\Omega + 1.5k\Omega) = 18.274V$$

Multisim Voltage Output

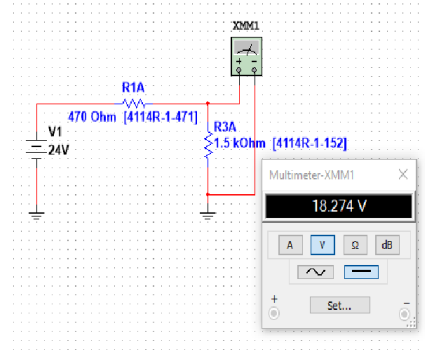

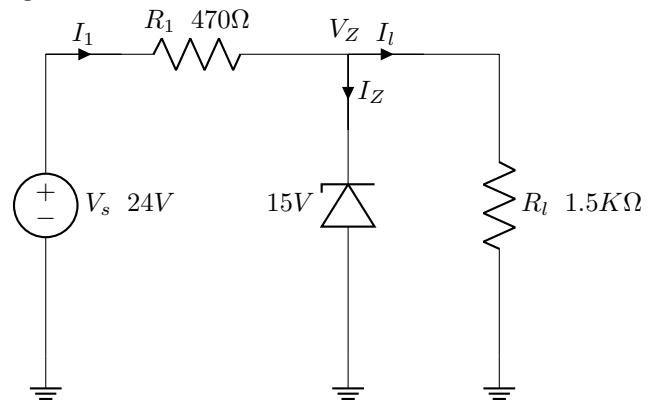**Question 12** calculate all three currents.




**Answer to Question 12**

$$I_1 = (V_s - V_z) / R_1 = 24V - 15V / 470\Omega = 19.2 \text{ mA}$$


$$I_L = V_z / R_L = 15V / 1.5k\Omega = 10 \text{ mA}$$

$$I_z = I_1 - I_L = 19.2 \text{ mA} - 10 \text{ mA} = 9.2 \text{ mA}$$

Multisim voltage output

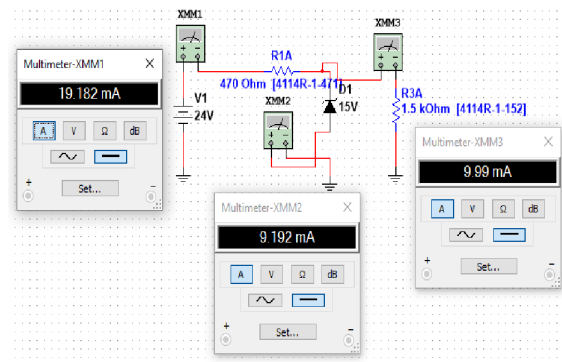

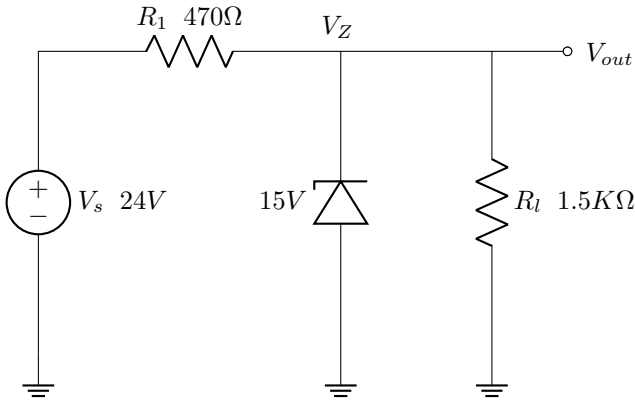**Question 13** The zener diode has a zener resistance of  $14\Omega$ . If the power supply has a ripple of  $1\text{v pp}$ , what is the ripple across load resistor.



**Answer to Question 13**

$$R_z = 12\Omega$$

$$R_s = 460\Omega$$

$$V_{\text{ripplein}} = 1\text{v pp}$$

$$V_{\text{rippleout}} = V_{\text{ripplein}} * R_z / (R_z + R_s)$$

$$V_{\text{rippleout}} = 1\text{vpp} * 12\Omega / (460\Omega + 12\Omega) = 28.9\text{ mV pp}$$

**Question 14** What is the current through the LED?

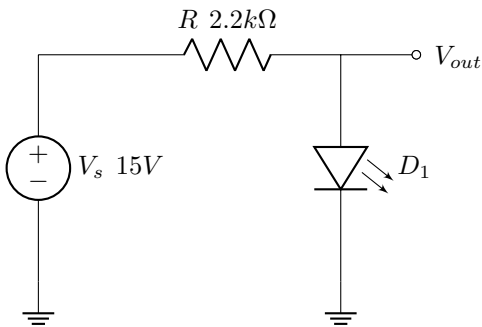


Fig 5-42


$$\text{Voltage drop on LED} = v_d = 2\text{V}$$

$$V_s = 15\text{V}$$

$$R = 2.2\text{ k}\Omega$$

$$I = (V_s - v_d) / R = (15\text{V} - 2\text{V}) / 2.2\text{ k}\Omega = 5.91\text{mA}$$

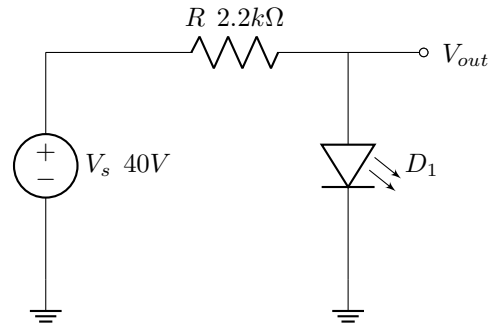**Question 15** if the supply voltage increases to  $40\text{V}$ , what is the LED current?




$$\text{voltage drop on LED} = V_d = 2\text{V}$$

$$V_s = 40\text{V}$$

$$R = 2.2\text{ k}\Omega$$


$$I = (V_s - v_d) / R = (40\text{V} - 2\text{V}) / 2.2\text{ k}\Omega = 17.28\text{mA}$$

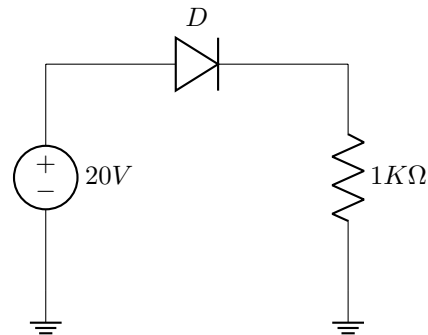**Question 16** Calculate the load current, load voltage, and total power. Assume the diode is ideal where forward voltage of diode is  $0\text{V}$ .



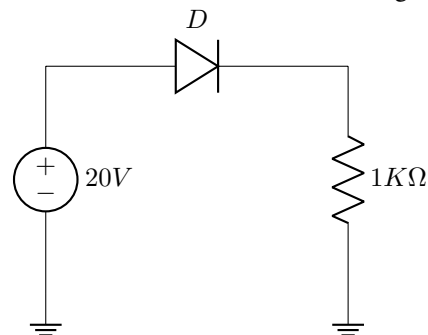**Answer to Question 16**

Diode is ideal where forward voltage of diode is  $0\text{V}$ .



$$\text{Load current} = I_l = 20\text{V} / 1\text{K}\Omega = 20\text{mA}$$

$$\text{Load voltage} = V_l = 20\text{mA} * 1\text{K}\Omega = 20\text{V}$$

$$\text{Load power} = P_l = I_l * V_l = 20\text{V} * 20\text{mA} = 400\text{mW}$$


$$\text{Total power} = P_l + P_d$$

Since diode is ideal forward voltage of diode is 0V, so the power through diode is

$$P_d = V_d * I = 0\text{V} * 20\text{mA} = 0\text{W}$$


$$\text{Total power} = P_l + P_d = 400\text{mW} + 0\text{W} = 400\text{mW}$$

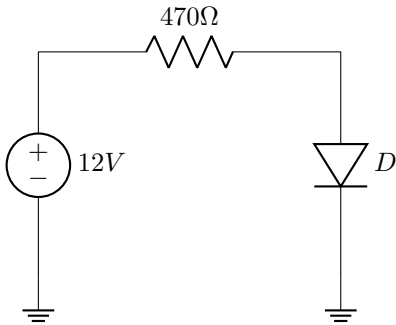**Question 17** If the resistor is double, what is the load current? Assume the diode is ideal where forward voltage of diode is 0V.



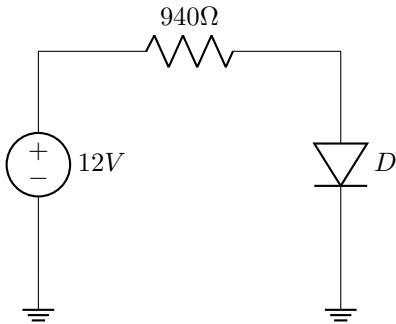**Answer to Question 17**


Since the resistor value is double new resistor value, new resistor value is  $2 * 470\Omega$ , which is  $940\Omega$



$$\text{Load current} = V_s / R$$

$$12\text{V} / 940\Omega = 12.8\text{mA}$$

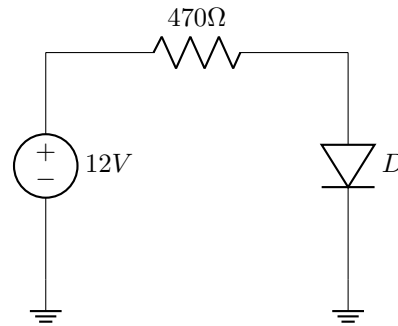**Question 18** Calculate load current, load voltage, load power, diode power, and total power.



**Answer to Question 18**

In second approximation, the diode is not ideal. Assuming that temperature is in  $25^\circ\text{C}$ , the forward voltage of diode is 0.7V

Since  $V_s > 0.7\text{V}$ , it is forward bias

$$V_l = V_s - V_d$$

$$V_l = 12\text{V} - 0.7\text{V}$$

$$V_l = 11.3\text{V}$$


$$\text{Load current} = I_L = V_l / R_l = 11.3\text{V} / 470\Omega = 24.04\text{mA}$$

$$\text{Load power} = P_L = I_L * V_L = 11.3\text{V} * 24.04\text{mA} = 271.68\text{ mW}$$

$$\text{Diode Power} = P_d = V_d * I_d = 0.7\text{V} * 24.04\text{mA} = 16.828\text{mW}$$

$$\text{Total Power} = \text{Load power} + \text{Diode Power} = 271.68\text{ mW} + 16.828\text{mW} = 288.508\text{mW}.$$

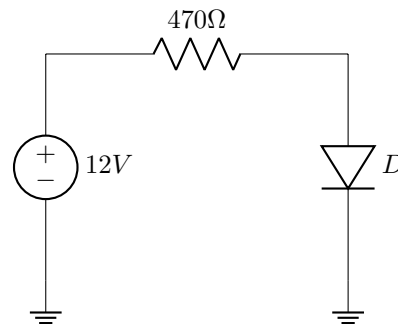
**Question 19** If the resistor is double, what is the load current?



**Answer to Question 19**

Resistor value is doubled so new resistor value is  $940\Omega$

Modified Circuit

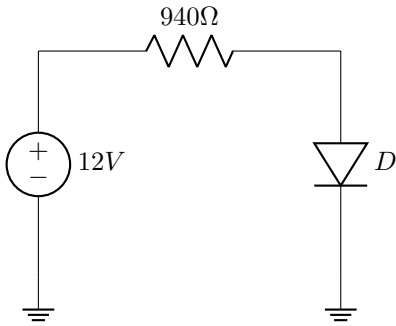

Diode is not ideal in second approximation. Assuming that temperature is in 25C, the forward voltage of diode is 0.7V

$$V_s = 12V$$

Since  $V_s > 0.7V$ , diode is in forward bias

$$V_l = V_s - V_d$$

$$V_l = 12V - 0.7V$$

$$V_l = 11.3V$$

$$\text{Load current} = I_L = V_l / R_l = 11.3V / 940\Omega = 12.02mA$$

$$V_l = 11.3V$$

$$\text{Load current} = I_L = V_l / R_l = 11.3V / 470.23\Omega = 24.0309mA$$

$$\text{Load power} = P_L = I_L * V_L = 11.3V * 24.0309mA = 271.5492mW$$

$I_L = I_d$  because they are in series


$$\text{Diode Power} = P_d = V_d * I_d = 0.7V * 24.0309mA = 16.8216mW$$

$$\begin{aligned} \text{Total Power} &= \text{Load power} + \text{Diode Power} = 271.5492mW + 16.8216mW \\ &= 288.37mW. \end{aligned}$$

**Question 20** Calculate the load current, load voltage, load power, diode power, and total power.  $R_B = 0.23\Omega$
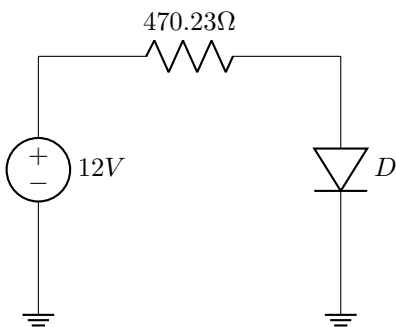
### Answer to Question 20

Since bulk resistance is in series in  $470\Omega$  the equivalent resistance is  $470.23\Omega$



Diode is not ideal in third approximation. Assuming that temperature is in 25C, the forward voltage of diode is 0.7V


Since  $V_s > 0.7V$ , it is forward bias

$$V_l = V_s - V_d$$

$$V_l = 12V - 0.7V$$




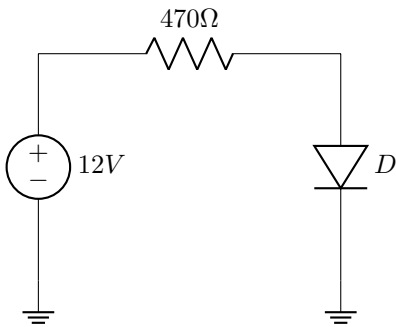**Question 21** If the diode polarity is reversed, what is the diode current? The diode voltage?



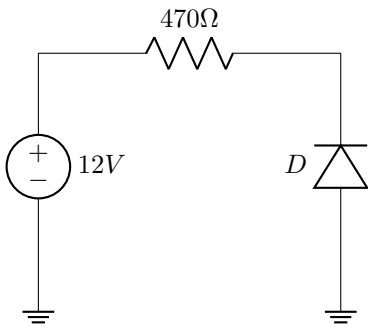**Answer to Question 21**

Diode polarity is reversed. So modified circuit is



Since diode polarity is reversed. The diode is in reverse biased. This means the diode will act as open circuit. As diode being open circuit, the current through the circuit is 0A. Since there is no current flowing, the voltage of bus above the diode is 12V, and below the bus of the diode is 0 v(Since it is grounded).

Thus, the voltage across diode is 12V. and current through diode is 0A because it acts as open circuit when it is reversed biased.