

Operational Amplifier

Jiwook Kim

1 The input voltage to an op amp is a large voltage step. The output is an exponential waveform that changes 2.0 V in 0.4 μ s. What is the slew rate of the op amp?

$$\Delta V_{out} = 2V$$

$$\Delta t = 0.4 \mu s$$

$$S_R = (\Delta V_{out}) / (\Delta t) = 5 V/\mu s$$

2 Use Eq. (16-2) to calculate the power bandwidth for each of the following:

a. $S_R = 0.5 V/\mu s$ and $V_p = 1 V$

$$f_{max} = S_R / (2\pi * V_p) = 0.5 V/\mu s / (2\pi * 1V) = 80kHz$$


b. $S_R = 3 V/\mu s$ and $V_p = 5 V$

$$f_{max} = S_R / (2\pi * V_p) = 3 V/\mu s / (2\pi * 5V) = 95.5kHz$$

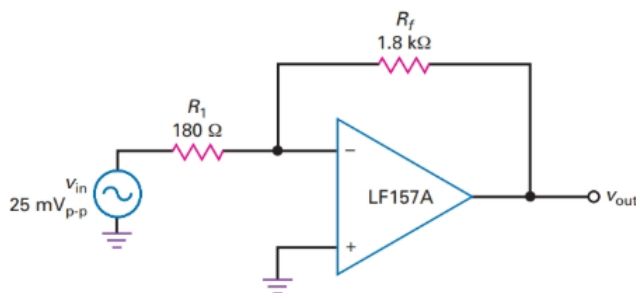c. $S_R = 15 V/\mu s$ and $V_p = 10V$

$$f_{max} = S_R / (2\pi * V_p) = 15 V/\mu s / (2\pi * 10V) = 238.7kHz$$

3 What are the closed-loop voltage gain and bandwidth in Fig. 16-30? What is the output voltage at 1 kHz? At 10 MHz? Draw the ideal Bode plot of closed-loop voltage gain.



Inverting Amplifier

$$A = -R_f / R_1 = -1.8k\Omega / 180\Omega = -10$$

Calculate the bandwidth

$$f_2 = \text{unity gain frequency} / (A_V) = 1\text{Mhz} / 10 = 100\text{Khz}$$

$$A_{vcl(db)} = 20 * \log(A_{VCL}) = 20 \log 10 = 20\text{db}$$

at 1 Mhz A_V is = 0db

AT 1Khz

$$V_{out} = A_{VCL} * V_{in} = -10 * 25\text{mv} = -250\text{mV pp}$$

Calculate the gain at 10MHZ

Slope is -20db/dec and $A_{VCL1\text{mhz}}$ is 0.

$$A_{VCL10\text{mhz}(db)} = A_{VCL1\text{mhz}} + -20 * (\log(10\text{mhz}/1\text{mhz}))$$

$$A_{VCL10\text{mhz}(db)} = 0 - 20 * 1$$


$$A_{VCL10\text{mhz}(db)} = -20 \text{ db}$$

$$A_{VCL10\text{mhz}} = 10^{(A_{VCL10\text{mhz}(db)}/20)} = 0.1$$

voltage gain is 0.1

$$V_{out} = 0.1 (V_{in}) = 0.1 * 25\text{mV} = 2.5\text{mV pp}$$

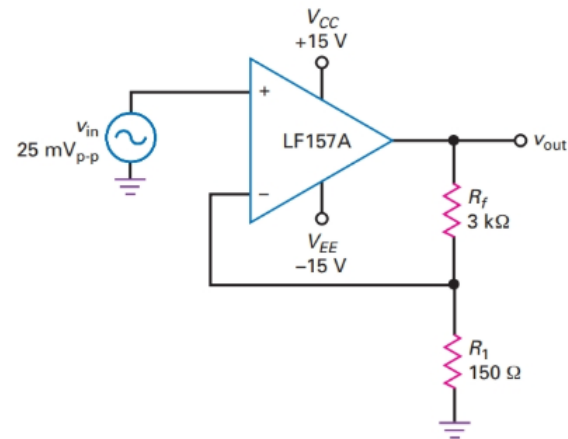4 In Fig. 16-32, what are the closed-loop voltage gain and bandwidth? The ac output volt-age at 100 kHz?



Non inverting amplifier. $A = 1 + R_f / R_1$

$$A_{VCL} = 1 + 3k\Omega / 150\Omega = 1 + 20 = 21$$

Unity gain frequency 1MHZ

$$f_2 = \text{unity gain frequency} / (A_V) = 1\text{Mhz} / 21 = 47\text{Khz}$$

$$A_{VCLdb} = 20\log(A_{VCL}) = 20 \log 21 = 26.44\text{dB}$$

it is down 20db in 100khz, which means that it is 6.44db in 100khz


$$A_{VCL100\text{khz}} = 10^{(6.44/20)} = 2.1$$

$$v_{out} = 2.1 * v_{in}$$

$$v_{out} = 2.1 * 25\text{mV pp} = 52.5\text{ mV pp}$$

At 100 kHz v_{out} is 52.5mV pp

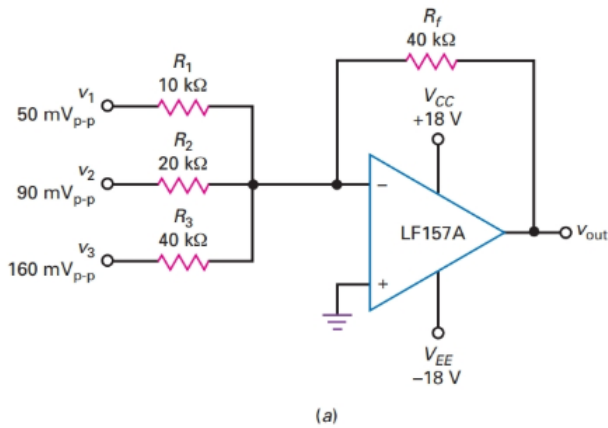5 In Fig. 16-33a, what is the ac output voltage? If a compensating resistor needs to be added to the non inverting input, what size should it be



inverting amplifier with summation

$$A1 = -r_f/r_1 = -40\text{k}\Omega/R_1 = -40\text{k}\Omega/10\text{k}\Omega = -4$$

$$A2 = -r_f/r_1 = -40\text{k}\Omega/R_1 = -40\text{k}\Omega/20\text{k}\Omega = -2$$


$$A3 = -r_f/r_1 = -40\text{k}\Omega/R_1 = -40\text{k}\Omega/40\text{k}\Omega = -1$$

$$V_{out} = A1*50\text{mV} + A2*90\text{mV} + A3*160\text{mV} = -540\text{mVPP}$$

Compensating resistor

$$R_{b2} = 10\text{k}\Omega || 20\text{k}\Omega || 40\text{k}\Omega || 40\text{k}\Omega = 5\text{k}\Omega$$

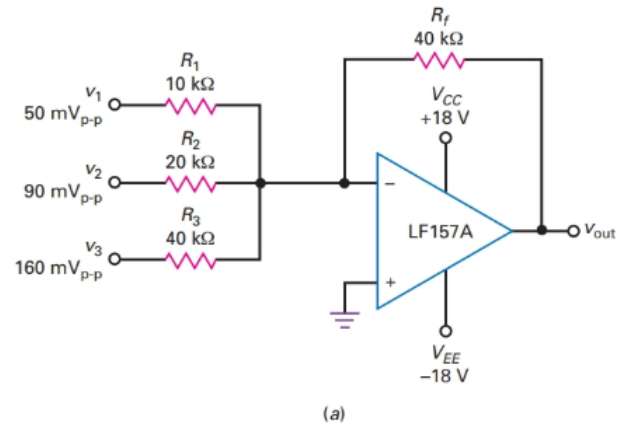6 If the feedback resistor in Fig. 16-33a is changed to a 100kΩ variable resistor, what is the maximum output voltage? The minimum?



Minimum resistance when $R_f=0$
the circuit act as voltage follower hence,

$$v_{out} = v_{in1} + v_{in2} + v_{in3} = 50\text{mV} + 90\text{mV} + 160\text{mV} = 300\text{mV}$$

When $R_f=100\text{k}\Omega$

inverting amplifier with summation

$$A1 = -r_f/r_1 = -100\text{k}\Omega/R_1 = -100\text{k}\Omega/10\text{k}\Omega = -10$$

$$A2 = -r_f/r_1 = -100\text{k}\Omega/R_1 = -100\text{k}\Omega/20\text{k}\Omega = -5$$


$$A3 = -r_f/r_1 = -100\text{k}\Omega/R_1 = -100\text{k}\Omega/40\text{k}\Omega = -2.5$$

$$V_{out} = A1*50\text{mV} + A2*90\text{mV} + A3*160\text{mV} = -1.35\text{V pp}$$

$$V_{outmax} = -1.35\text{V pp}$$

$$V_{outmin} = 300\text{mV pp}$$

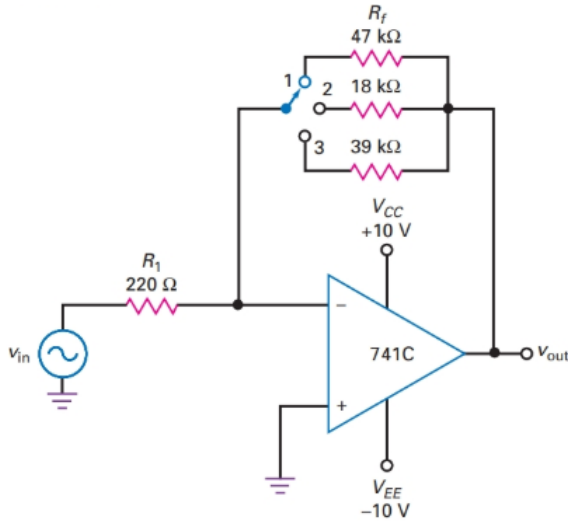7 In Fig. 16-36, what is the closed-loop voltage gain for each switch position?



Inverting Amplifier


$$A_{v(cl)} = -R_f/r_1 = -R_f/220\Omega$$

$$A_{v(cl1)} = -47\text{k}\Omega/220\Omega = -213.6$$

$$A_{v(cl2)} = -18\text{k}\Omega/220\Omega = -81.8$$

$$A_{v(cl3)} = -39\text{k}\Omega/220\Omega = -177.3$$

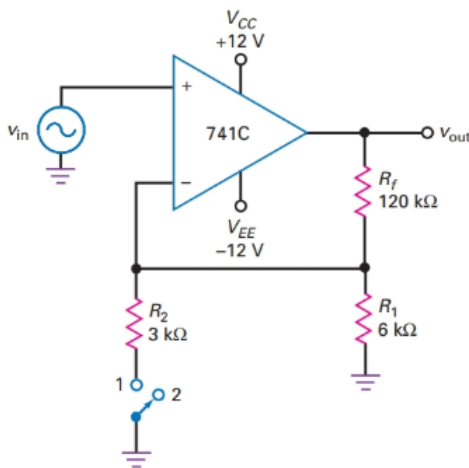8 What is the closed-loop voltage gain for each switch position of Fig. 16-37? The bandwidth?



Closed loop voltage gain

$$A_{v(cl)} = R_f/r_1 + 1 = 120\text{k}\Omega/6\text{k}\Omega + 1 = 21$$

$$f_{unity} = 1\text{Mhz}$$

$$f_{2cl} = 1\text{Mhz}/A_{v(cl)} = 47.6\text{khz}$$

When switch is on.


$$R_1 = 3\text{k}\Omega \parallel 6\text{k}\Omega = 2\text{k}\Omega$$

$$A_{v(cl)} = R_f/r_1 + 1 = 120\text{k}\Omega/2\text{k}\Omega + 1 = 61$$

$$f_{unity} = 1\text{Mhz}$$

$$f_{2cl} = 1\text{Mhz}/A_{v(cl)} = 16.4\text{khz}$$

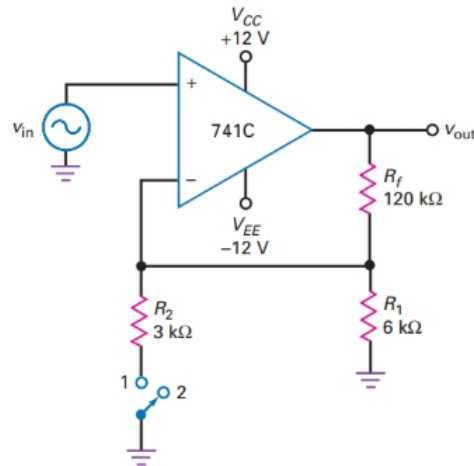9 If the 120-kΩ resistor opens in Fig. 16-37, what is the output voltage most likely to do



This is non inverting amplifier


$$A_{Vcl} = R_f/r_1 + 1$$

As Rf opens its infinity, thus, there is no feedback. So the output of the opamp keeps on increasing and goes to saturation with limit -12V to 12V

Thus the output voltage will go to positive or negative saturation.

10 What is the closed-loop voltage gain for each switch position of Fig. 16-38? The bandwidth?

Figure 16-38

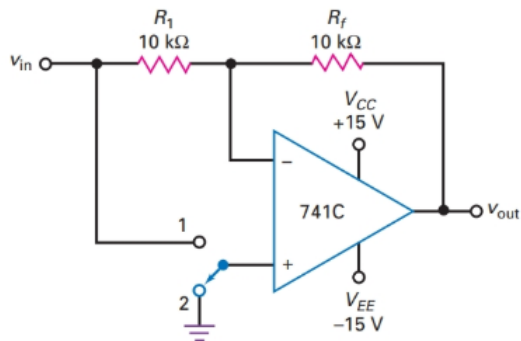

if switch is connected to 1. $v_{out} = v_{in}$.

This is because current through R_1 is zero, as node left and right voltage is equal to v_{in} . This makes current through R_f is 0, thus, v_{out} equals to v_{in}

Thus, $A_v = 1$

bandwidth is

$$f_{2cl} = f_{unity} / A_v = 1 \text{ Mhz}$$

If switch is connected to 0. This is inverting amplifier

$$A = -R_f / R_1 = -1$$

$$f_{2cl} = f_{unity} / (|A_v| + 1) = 1 \text{ Mhz} / (1 + 1) = 500 \text{ KHz}$$