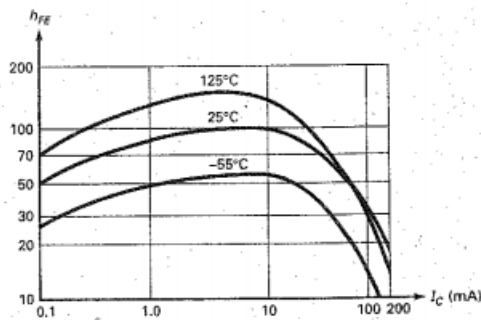


# Transistor Fundamentals

Jiwook Kim

**Question 1** Refer to Fig 7-1. What is the current gain of a 2N3904 when the collector current is 100mA and the junction temperature is 125°C?

Figure 7-1 Variation of current gain.




Chapter 7

According to Fig 1, For 2N3904, when collector current is 100mA and junction temperature is 125C, current gain is 30

$$H_{FE} = 30$$

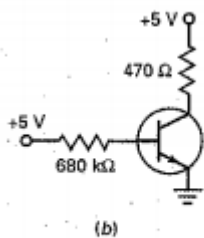**Question 2.** The resistors of Fig. 7-25a have a tolerance of  $\pm 5$  percent The supply voltages have a tolerance of  $\pm 10$  percent If the current gain can vary from 50 to 150, what is the minimum possible voltage from collector to ground?



$$I_B = (V_{BB} - 0.7V)/R_B$$

$$V_C = V_{CC} - I_C * R_C = V_{CC} - I_B * \beta * R_C = V_{CC} - (V_{BB} - 0.7V) / R_B * \beta * R_C$$

$$\text{Thus, } V_C = V_{CC} - (V_{BB} - 0.7V) / R_B * \beta * R_C$$

$$V_{Cmax} = V_{CC(max)} - (V_{BB(min)} - 0.7V) / R_{B(max)} * \beta_{min} * R_{C(min)}$$

$$V_{Cmin} = V_{CC(min)} - (V_{BB(max)} - 0.7V) / R_{B(min)} * \beta_{max} * R_{C(max)}$$

$$V_{CC(min)} = 0.90 * V_{CC} = 4.5V$$

$$V_{CC(max)} = 1.10 * V_{CC} = 5.5V$$

$$V_{BB(min)} = 0.90 * V_{BB} = 4.5V$$

$$V_{BB(max)} = 1.10 * V_{BB} = 5.5V$$

$$R_{B(min)} = 0.95 * R_B = 646k\Omega$$

$$R_{B(max)} = 1.05 * R_B = 714k\Omega$$

$$R_{C(min)} = 0.95 * R_C = 446.5\Omega$$

$$R_{C(max)} = 1.05 * R_C = 493.5\Omega$$

$$\beta_{(min)} = 50$$

$$\beta_{(max)} = 150$$

Applying

$$V_{C(max)} = V_{CC(max)} - (V_{BB(min)} - 0.7V) / R_{B(max)} * \beta_{(min)} * R_{C(min)} = 5.38V$$

$$V_{C(min)} = V_{CC(min)} - (V_{BB(max)} - 0.7V) / R_{B(min)} * \beta_{(max)} * R_{C(max)} = 3.95V$$

Figure 7-26



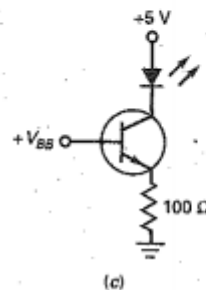
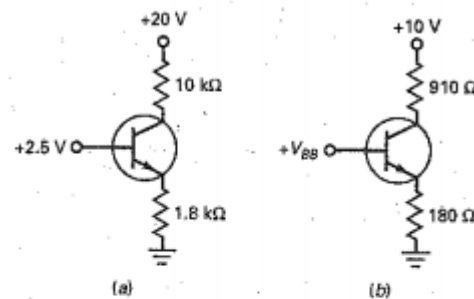
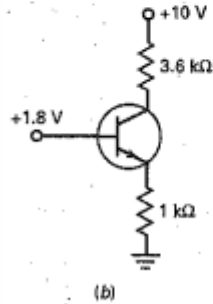


Figure 7-27

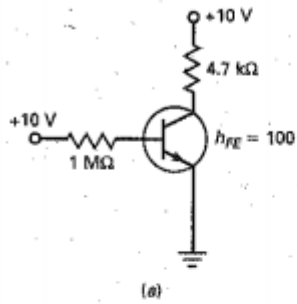


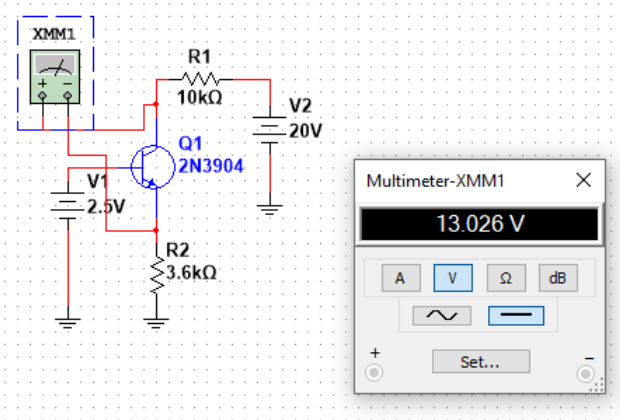**Question 3.**(Multisim) If the emitter resistor is doubled in fig 7-26a what is the collector-emitter voltage?




$$V_{CE} = 13V$$

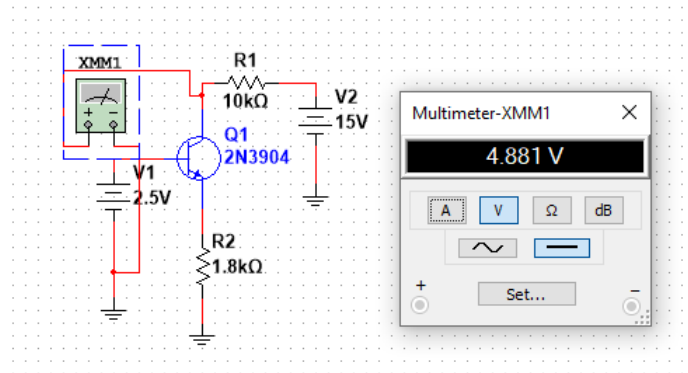**Question 4.** (Multisim) If the collector supply voltage is decreased to 15V in Fig 7-26a, what is the collector voltage?




$$V_C = 4.88V$$

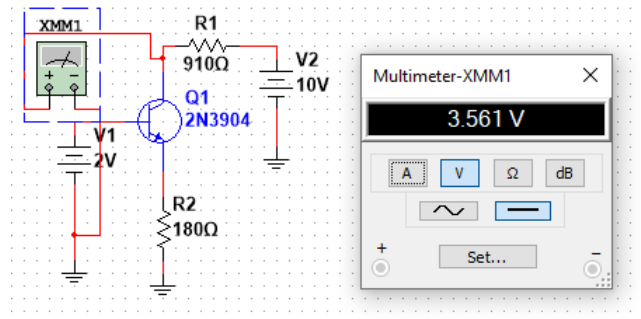**Question 5.** (Multisim)What is the collector voltage in Fig. 7-26b if  $V_{bb} = 2V$ ?



$$V_C = 3.56V$$

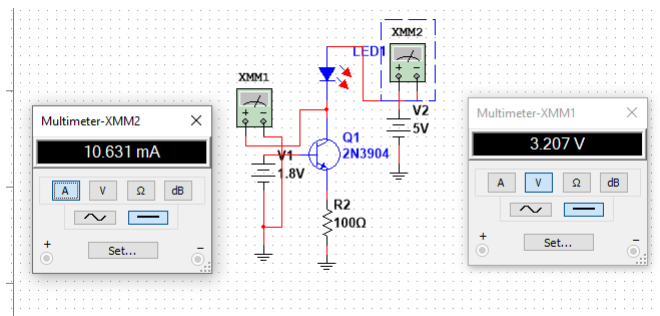**Question 6.** (Multisim) If  $V_{BB} = 1.8V$  in Fig 7-26C, what is the LED current? The appropriate  $V_C$ ?



$$I_C = 3.2V$$

$$V_C = 10.6mA$$

**Question 7.** The base supply voltage of Fig. 7-27a decreases by 10 percent. What happens to the base current, collector current, and collector voltage?

Base current

$$I_B = (V_{BB} - 0.7V)/R_B$$

Collector current

$$I_C = I_B * \beta$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C$$

Considering  $V_{BB} = 10V, V_{CC} = 10V$

Base current

$$I_B = (V_{BB} - 0.7V)/R_B = (10V - 0.7V)/1M\Omega = 9.3\mu A$$

Collector current

$$I_C = I_B * \beta = 9.3\mu A * 100 = 0.93mA$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 10V - 0.93mA * 4.7k\Omega = 5.629V$$

Considering  $V_{BB} = 9V$

Base current

$$I_B = (V_{BB} - 0.7V)/R_B = (9V - 0.7V)/1M\Omega = 8.3\mu A$$

Base current decreases as base supply voltage decreases.

Collector current

$$I_C = I_B * \beta = 8.3\mu A * 100 = 0.83mA$$

Collector current decreases as base supply voltage decreases.

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 10V - 0.83mA * 4.7k\Omega = 6.1V$$

Collector voltage Increases as base supply voltage decreases.

**Question 8.** The collector resistance of Fig. 7-27b increases by 10 percent. What happens to the emitter current, collector current, and collector voltage?

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E$$

Collector current

$$I_C = I_E * \beta$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C$$

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E = (1.8V - 0.7V)/1k\Omega = 1.1mA$$

Collector current

$$I_C \approx I_E = 1.1mA$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 10V - 1.1mA * 3.6k\Omega = 6.04V$$

Considering Collector resistance increase by 10 percent

$$R_C = 3.96k\Omega$$

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E = (1.8V - 0.7V)/1k\Omega = 1.1mA$$

Emitter current remains the same as collector resistance increase

$$I_C \approx I_E = 1.1mA$$

Collector current remains the same as collector resistance increase

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 10V - 1.1mA * 3.96k\Omega = 5.644V$$

Collector voltage decreases as collector resistance increase

**Question 9.** The collector supply voltage of Fig. 7-27b increases by 10 percent. What happens to the emitter current, collector current, and collector voltage?

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E$$

Collector current

$$I_C = I_E * \beta$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C$$

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E = (1.8V - 0.7V)/1k\Omega = 1.1mA$$

Collector current

$$I_C \approx I_E = 1.1mA$$

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 10V - 1.1mA * 3.6k\Omega = 6.04V$$

supply voltage increase by 10 percent

$$V_{CC} = 11V$$

Emitter current

$$I_E = (V_{BB} - 0.7V)/R_E = (1.8V - 0.7V)/1k\Omega = 1.1mA$$

Emitter current remains the same as collector supply voltage increase

$$I_C \approx I_E = 1.1mA$$

Collector current remains the same as collector supply voltage increase

Collector voltage

$$V_C = V_{CC} - I_C * R_C = 11V - 1.1mA * 3.6k\Omega = 7.04V$$

Collector voltage increases as supply voltage increase

**Question 10.** What if the ground on the emitter is open in Fig. 7-27a? What will a voltmeter read for the base voltage? For the collector voltage?

If the ground on emitter is open

Base voltage will remain the same because it is sending 10V, Based voltage is 10V Which is  $V_{BB}$

Since there are no current flowing through the circuit.  $I_C$  will equal to zero, Using the kirchhoff's voltage law  $V_C = V_{CC} - I_C * R_C$ , Since  $I_C$  is zero,  $V_C$  will equal to  $V_{CC}$  which is 10V.

Collector voltage = 10V which is  $V_{CC}$